

# Processor Architecture III: Sequential Implementation

Kai Zhang  
Fudan University  
[zhangk@fudan.edu.cn](mailto:zhangk@fudan.edu.cn)

# Y86-64 Instruction Set #1

Byte	0	1	2	3	4	5	6	7	8	9
halt	0	0								
nop	1	0								
cmovXX rA, rB	2	fn	rA	rB						
irmovq V, rB	3	0	F	rB	V					
rmmovq rA, D(rB)	4	0	rA	rB	D					
mrmovq D(rB), rA	5	0	rA	rB	D					
OPq rA, rB	6	fn	rA	rB						
jXX Dest	7	fn	Dest							
call Dest	8	0	Dest							
ret	9	0								
pushq rA	A	0	rA	F						
popq rA	B	0	rA	F						

# Y86-64 Instruction Set #2

Byte	0	1	2	3	4	5	6															
halt	0	0						{ <ul style="list-style-type: none"> <li>rrmovq <table border="1" style="display: inline-table; vertical-align: middle;"><tr><td>2</td><td>0</td></tr></table></li> <li>cmovle <table border="1" style="display: inline-table; vertical-align: middle;"><tr><td>2</td><td>1</td></tr></table></li> <li>cmovl <table border="1" style="display: inline-table; vertical-align: middle;"><tr><td>2</td><td>2</td></tr></table></li> <li>cmove <table border="1" style="display: inline-table; vertical-align: middle;"><tr><td>2</td><td>3</td></tr></table></li> <li>cmovne <table border="1" style="display: inline-table; vertical-align: middle;"><tr><td>2</td><td>4</td></tr></table></li> <li>cmovge <table border="1" style="display: inline-table; vertical-align: middle;"><tr><td>2</td><td>5</td></tr></table></li> <li>cmovg <table border="1" style="display: inline-table; vertical-align: middle;"><tr><td>2</td><td>6</td></tr></table></li> </ul> }	2	0	2	1	2	2	2	3	2	4	2	5	2	6
2	0																					
2	1																					
2	2																					
2	3																					
2	4																					
2	5																					
2	6																					
nop	1	0																				
cmovXX rA, rB	2	fn	rA	rB																		
irmovq V, rB	3	0	F	rB	V																	
rmmovq rA, D(rB)	4	0	rA	rB	D																	
mrmovq D(rB), rA	5	0	rA	rB	D																	
OPq rA, rB	6	fn	rA	rB																		
jXX Dest	7	fn	Dest																			
call Dest	8	0	Dest																			
ret	9	0																				
pushq rA	A	0	rA	F																		
popq rA	B	0	rA	F																		

# Y86-64 Instruction Set #3

Byte	0	1	2	3	4	5	6	7	8	9
halt	0	0								
nop	1	0								
cmovXX rA, rB	2	fn	rA	rB						
irmovq V, rB	3	0	F	rB	V					
rmmovq rA, D(rB)	4	0	rA	rB	D					
mrmovq D(rB), rA	5	0	rA	rB	D					
OPq rA, rB	6	fn	rA	rB						
jXX Dest	7	fn	Dest							
call Dest	8	0	Dest							
ret	9	0								
pushq rA	A	0	rA	F						
popq rA	B	0	rA	F						

addq	6	0
subq	6	1
andq	6	2
xorq	6	3

*Note: An arrow points from the 'fn' field of the OPq instruction to the 'fn' field of the addq, subq, andq, and xorq instructions.*


# Y86-64 Instruction Set #4

Byte	0	1	2	3	4	5	6	7				
halt	0	0								jmp	7	0
nop	1	0								jle	7	1
cmovXX rA, rB	2	fn	rA	rB						j1	7	2
irmovq V, rB	3	0	F	rB	V					je	7	3
rmmovq rA, D(rB)	4	0	rA	rB	D					jne	7	4
mrmovq D(rB), rA	5	0	rA	rB	D					jge	7	5
OPq rA, rB	6	fn	rA	rB						jg	7	6
jXX Dest	7	fn	Dest									
call Dest	8	0	Dest									
ret	9	0										
pushq rA	A	0	rA	F								
popq rA	B	0	rA	F								

# Building Blocks

 
## ■ Combinational Logic

- Compute Boolean functions of inputs
- Continuously respond to input changes
- Operate on **data** and implement **control**


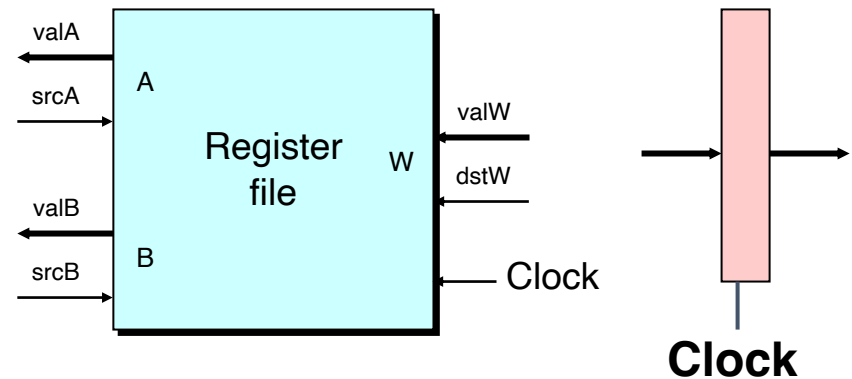
## ■ Storage Elements

- Store bits
- Addressable **memories**
- Non-addressable **registers**
- Loaded only as clock rises



# Hardware Control Language

- Very simple hardware description language
- Can only express limited aspects of hardware operation
  - Parts we want to explore and modify

## ■ Data Types

- `bool`: Boolean
  - `a, b, c, ...`
- `int`: words
  - `A, B, C, ...`
  - Does not specify word size---bytes, 32-bit words, ...

## ■ Statements

- `bool a = bool-expr ;`
- `int A = int-expr ;`

# HCL Operations

- Classify by type of value returned

## ▪ Boolean Expressions

### ▪ Logic Operations

- `a && b, a || b, !a`

### ▪ Word Comparisons

- `A == B, A != B, A < B, A <= B, A >= B, A > B`

### ▪ Set Membership

- `A in { B, C, D }`
  - Same as `A == B || A == C || A == D`

## ▪ Word Expressions

### ▪ Case expressions

- `[ a : A; b : B; c : C ]`
- Evaluate test expressions `a, b, c, ...` in sequence
- Return word expression `A, B, C, ...` for first successful test



# How to implement hardware?

- **Map to a 2-D integrated circuits: Cost**
- **Minimum number of hardware units**
- **Simple and consistent structure**
  - One ALU
- **Similar procedure for all instructions**


# SEQ Hardware Structure

## State

- Program counter register (PC)
- Condition code register (CC)
- Register File
- Memories
  - Access same memory space
  - Data: for reading/writing program data
  - Instruction: for reading instructions

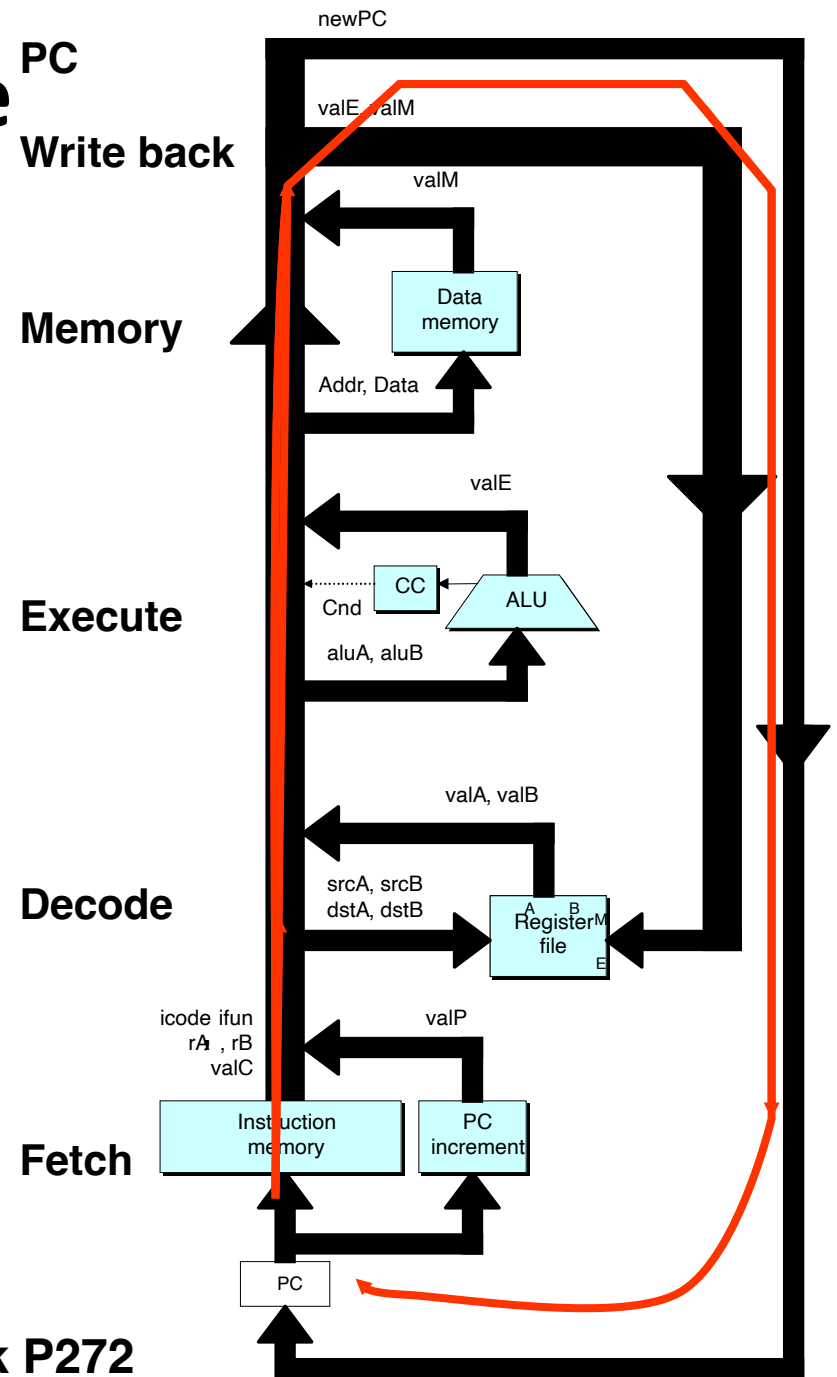
## Instruction Flow

- Read instruction at address specified by PC
- Process through stages
- Update program counter






# Instruction Decoding

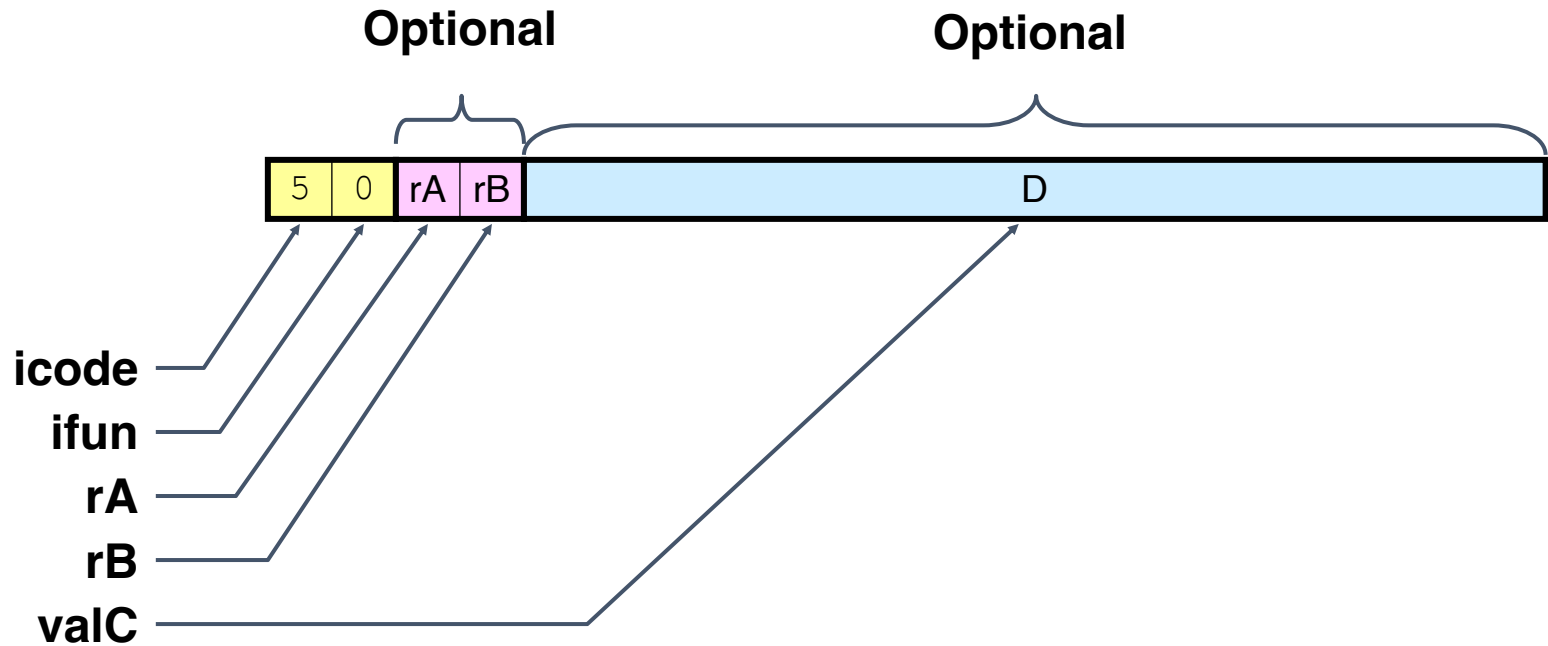

## ■ Instruction Format

- Instruction byte      icode:ifun
- Optional register byte      rA:rB
- Optional constant word      valC

# Executing Arith./Logical Operation

 

## ▪ Fetch

- Read 2 bytes

## ▪ Decode

- Read operand registers

## ▪ Execute

- Perform operation
- Set condition codes

## ▪ Memory

- Do nothing

## ▪ Write back

- Update register

## ▪ PC Update

- Increment PC by 2

# Stage Computation: Arith/Log. Ops

	OPq rA, rB	
Fetch	icode:ifun $\leftarrow$ M <sub>1</sub> [PC] rA:rB $\leftarrow$ M <sub>1</sub> [PC+1]	Read instruction byte Read register byte
	valP $\leftarrow$ PC+2	Compute next PC
Decode	valA $\leftarrow$ R[rA]	Read operand A
	valB $\leftarrow$ R[rB]	Read operand B
Execute	valE $\leftarrow$ valB OP valA	Perform ALU operation
	Set CC	Set condition code register
Memory		
Write back	R[rB] $\leftarrow$ valE	Write back result
	PC update	PC $\leftarrow$ valP

- Formulate instruction execution as sequence of simple steps
- Use same general form for all instructions

# Executing `rmmovq`

`rmmovq rA, D(rB)`



## Fetch

- Read 10 bytes

## Decode

- Read operand registers

## Execute

## Memory

## Write back

## PC Update

# Executing `rmmovq`

`rmmovq rA, D(rB)`

4	0	rA	rB
---	---	----	----

D

## Fetch

- Read 10 bytes

## Decode

- Read operand registers

## Execute

- Compute effective address

## Memory

- Write to memory

## Write back

- Do nothing

## PC Update

- Increment PC by 10



# Stage Computation: `rmmovq`

	<code>rmmovq rA, D(rB)</code>	
Fetch	$icode:ifun \leftarrow M_1[PC]$ $rA:rB \leftarrow M_1[PC+1]$ $valC \leftarrow M_8[PC+2]$ $valP \leftarrow PC+10$	Read instruction byte Read register byte Read displacement D Compute next PC
Decode	$valA \leftarrow R[rA]$ $valB \leftarrow R[rB]$	Read operand A Read operand B
Execute	$valE \leftarrow valB + valC$	Compute effective address
Memory	$M_8[valE] \leftarrow valA$	Write value to memory
Write back		
PC update	$PC \leftarrow valP$	Update PC

- Use ALU for address computation

# Quiz Time!

## Exercise 4.13

# Executing popq



▪ Fetch

▪ Decode

▪ Execute

▪ Memory

▪ Write back

▪ PC Update

# Executing popq



## Fetch

- Read 2 bytes

## Decode

- Read stack pointer

## Execute

- Increment stack pointer by 8

## Memory

- Read from old stack pointer

## Write back

- Update stack pointer (`%rsp`)
- Write result to register

## PC Update

- Increment PC by 2

# Stage Computation: popq

	popq rA	
Fetch	icode:ifun $\leftarrow M_1[PC]$ rA:rB $\leftarrow M_1[PC+1]$	Read instruction byte Read register byte
	valP $\leftarrow PC+2$	Compute next PC
Decode	valA $\leftarrow R[\%rsp]$ valB $\leftarrow R[\%rsp]$	Read stack pointer Read stack pointer
	valE $\leftarrow valB + 8$	Increment stack pointer
Memory	valM $\leftarrow M_8[valA]$	Read from stack
Write back	R[%rsp] $\leftarrow valE$ R[rA] $\leftarrow valM$	Update stack pointer Write back result
	PC update	PC $\leftarrow valP$

- Use ALU to increment stack pointer
- Must update two registers
  - Popped value
  - New stack pointer

# Quiz Time!

**Exercise 4.14**

# Executing Conditional Moves

`cmovXX rA, rB`

2	fn	rA	rB
---	----	----	----

▪ Fetch

▪ Memory

▪ Decode

▪ Write back

▪ Execute

▪ PC Update

# Executing Conditional Moves

`cmovXX rA, rB`

2	fn	rA	rB
---	----	----	----

## Fetch

- Read 2 bytes

## Decode

- Read operand registers

## Execute

- If `!cnd`, then set destination register to `0xF`

## Memory

- Do nothing

## Write back

- Update register (or not)

## PC Update

- Increment PC by 2




# Stage Computation: Cond. Move

	<code>cmovXX rA, rB</code>	
Fetch	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$ $\text{rA:rB} \leftarrow M_1[\text{PC}+1]$	Read instruction byte Read register byte
	$\text{valP} \leftarrow \text{PC}+2$	Compute next PC
Decode	$\text{valA} \leftarrow R[\text{rA}]$ $\text{valB} \leftarrow 0$	Read operand A
Execute	$\text{valE} \leftarrow \text{valB} + \text{valA}$ If ! Cond(CC,ifun) $\text{rB} \leftarrow 0xF$	Pass valA through ALU (Disable register update)
Memory		
Write back	$R[\text{rB}] \leftarrow \text{valE}$	Write back result
PC update	$\text{PC} \leftarrow \text{valP}$	Update PC

- Read register rA and pass through ALU
- destination register to 0xF
  - If condition codeCancel move by setting s & move condition indicate no move

# Executing Jumps

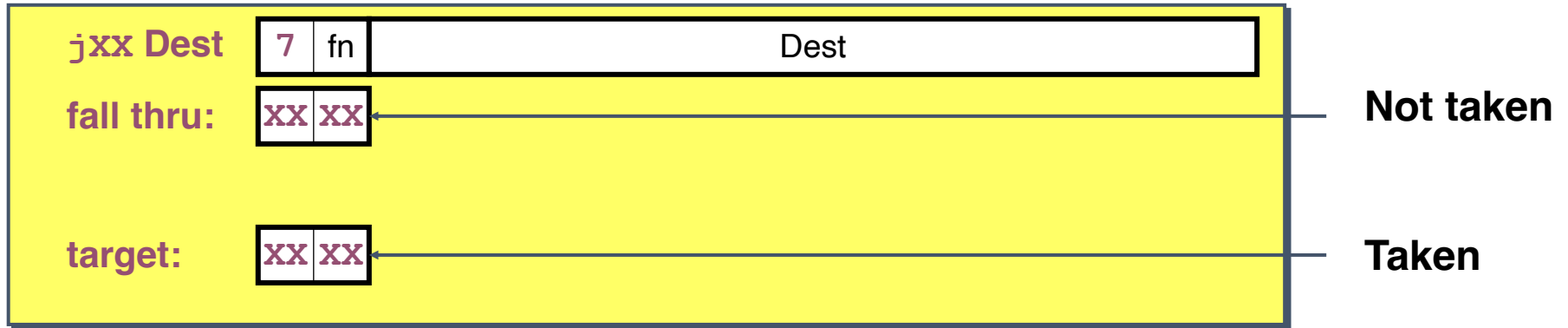

▪ Fetch

▪ Decode


▪ Execute

▪ Memory

▪ Write back

▪ PC Update

# Executing Jumps

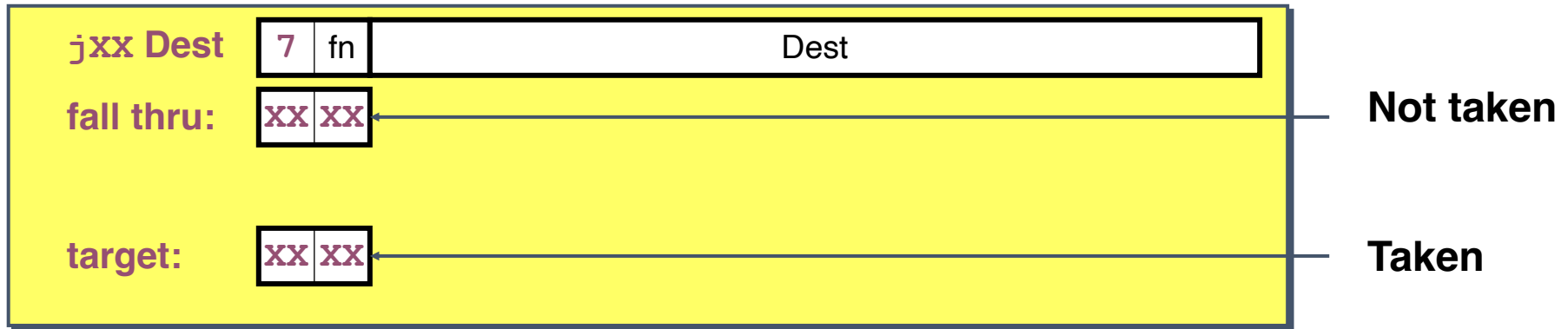

## Fetch

- Read 9 bytes
- Increment PC by 9

## Decode

- Do nothing

## Execute

- Determine whether to take branch based on jump condition and condition codes

## Memory

- Do nothing

## Write back

- Do nothing

## PC Update


- Set PC to Dest if branch taken or to incremented PC if not branch

# Stage Computation: Jumps

	jXX Dest	
Fetch	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$	Read instruction byte
	$\text{valC} \leftarrow M_8[\text{PC}+1]$	Read destination address
	$\text{valP} \leftarrow \text{PC}+9$	Fall through address
Decode		
Execute	$\text{Cnd} \leftarrow \text{Cond}(\text{CC}, \text{ifun})$	Take branch?
Memory		
Write back		
PC update	$\text{PC} \leftarrow \text{Cnd} ? \text{valC} : \text{valP}$	Update PC

- Compute both addresses
- Choose based on setting of condition codes and branch condition

# Executing call

 

▪ Fetch

▪ Decode


▪ Execute

▪ Memory

▪ Write back

▪ PC Update

# Executing call

 

## Fetch

- Read 9 bytes
- Increment PC by 9

## Decode

- Read stack pointer

## Execute

- Decrement stack pointer by 8

## Memory

- Write incremented PC to new value of stack pointer

## Write back

- Update stack pointer

## PC Update

- Set PC to Dest

# Stage Computation: call

	call Dest	
Fetch	$icode:ifun \leftarrow M_1[PC]$	Read instruction byte
	$valC \leftarrow M_8[PC+1]$	Read destination address
	$valP \leftarrow PC+9$	Compute return point
Decode	$valB \leftarrow R[\%rsp]$	Read stack pointer
Execute	$valE \leftarrow valB + -8$	Decrement stack pointer
Memory	$M_8[valE] \leftarrow valP$	Write return value on stack
Write back	$R[\%rsp] \leftarrow valE$	Update stack pointer
PC update	$PC \leftarrow valC$	Set PC to destination


- Use ALU to decrement stack pointer
- Store incremented PC

# Quiz Time!

**Exercise 4.18**



# Executing `ret`

 

▪ Fetch

▪ Decode


▪ Execute

▪ Memory

▪ Write back

▪ PC Update

# Executing `ret`

 

## Fetch

- Read 1 byte

## Decode

- Read stack pointer

## Execute

- Increment stack pointer by 8

## Memory

- Read return address from old stack pointer

## Write back

- Update stack pointer

## PC Update

- Set PC to return address

# Stage Computation: `ret`

ret		
Fetch	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$	Read instruction byte
Decode	$\text{valA} \leftarrow R[\%rsp]$ $\text{valB} \leftarrow R[\%rsp]$	Read operand stack pointer Read operand stack pointer
Execute	$\text{valE} \leftarrow \text{valB} + 8$	Increment stack pointer
Memory	$\text{valM} \leftarrow M_8[\text{valA}]$	Read return address
Write back	$R[\%rsp] \leftarrow \text{valE}$	Update stack pointer
PC update	$\text{PC} \leftarrow \text{valM}$	Set PC to return address

- Use ALU to increment stack pointer
- Read return address from memory

# Computation Steps

		OPq rA, rB	
Fetch	icode,ifun	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$	Read instruction byte
	rA,rB	$\text{rA:rB} \leftarrow M_1[\text{PC}+1]$	Read register byte
	valC		[Read constant word]
	valP	$\text{valP} \leftarrow \text{PC}+2$	Compute next PC
Decode	valA, srcA	$\text{valA} \leftarrow R[\text{rA}]$	Read operand A
	valB, srcB	$\text{valB} \leftarrow R[\text{rB}]$	Read operand B
Execute	valE	$\text{valE} \leftarrow \text{valB OP valA}$	Perform ALU operation
	Cond code	Set CC	Set/use cond. code reg
Memory	valM		[Memory read/write]
Write back	dstE	$R[\text{rB}] \leftarrow \text{valE}$	Write back ALU result
	dstM		[Write back memory result]
PC update	PC	$\text{PC} \leftarrow \text{valP}$	Update PC

- All instructions follow same general pattern
- Differ in what gets computed on each step

# Computation Steps

		call Dest	
Fetch	icode,ifun	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$ $\text{valC} \leftarrow M_8[\text{PC}+1]$ $\text{valP} \leftarrow \text{PC}+9$	Read instruction byte
	rA,rB		[Read register byte]
	valC		Read constant word
	valP		Compute next PC
Decode	valA, srcA	$\text{valB} \leftarrow R[\%rsp]$	[Read operand A]
	valB, srcB		Read operand B
Execute	valE	$\text{valE} \leftarrow \text{valB} + -8$	Perform ALU operation
	Cond code		[Set /use cond. code reg]
Memory	valM	$M_8[\text{valE}] \leftarrow \text{valP}$	Memory read/write
Write back	dstE	$R[\%rsp] \leftarrow \text{valE}$	Write back ALU result
	dstM		[Write back memory result]
PC update	PC	$\text{PC} \leftarrow \text{valC}$	Update PC

- All instructions follow same general pattern
- Differ in what gets computed on each step

# Computed Values

## ■ Fetch

icode	Instruction code
ifun	Instruction function
rAInstr.	Register A
rBInstr.	Register B
valC	Instruction constant
valP	Incremented PC

## ■ Decode

srcA	Register ID A
srcB	Register ID B
dstE	Destination Register E
dstM	Destination Register M
valA	Register value A
valB	Register value B

## ■ Execute

■ valE	ALU result
■ Cnd	Branch/move flag


## ■ Memory

■ valM	Value from memory
--------	-------------------


# SEQ Hardware
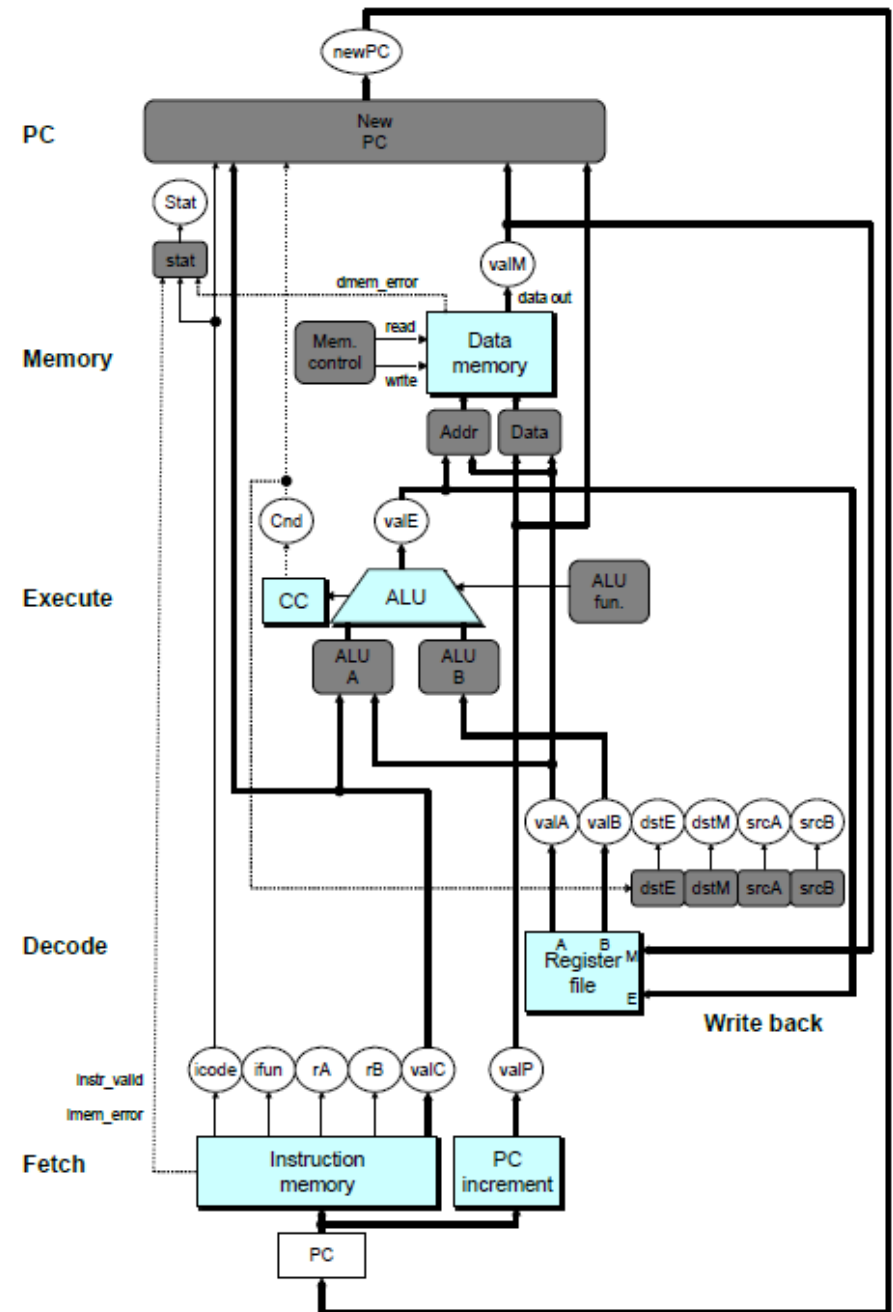
## Key

- Blue boxes: predesigned hardware blocks
  - E.g., memories, ALU
- Gray boxes: control logic
  - Describe in HCL
- White ovals: labels for signals
- Thick lines: 64-bit word values
- Thin lines: 4-8 bit values
- Dotted lines: 1-bit values



# Fetch Logic

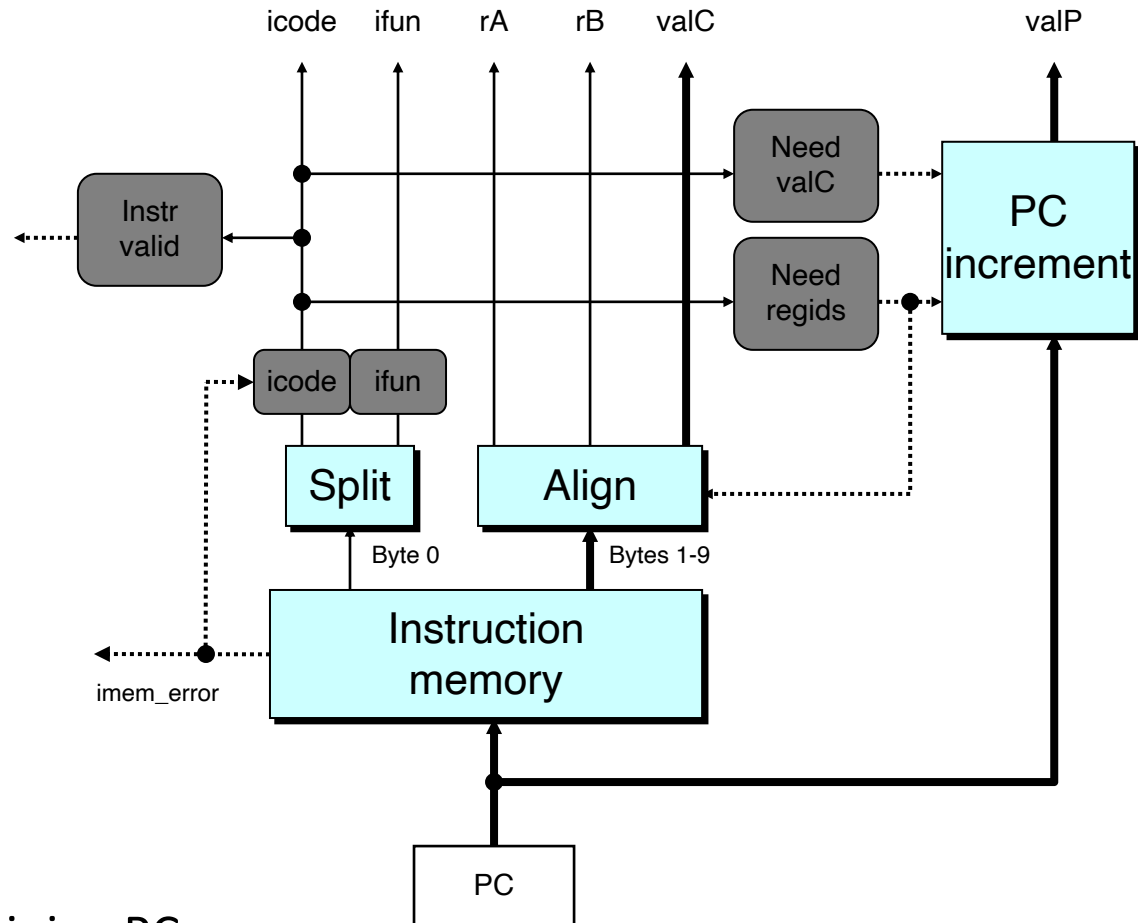


## ■ Predefined Blocks

- **PC**: Register containing PC
- **Instruction memory**: Read 10 bytes (PC to PC+9)
  - Signal invalid address
- **Split**: Divide instruction byte into icode and ifun
- **Align**: Get fields for rA, rB, and valC



# Fetch Logic

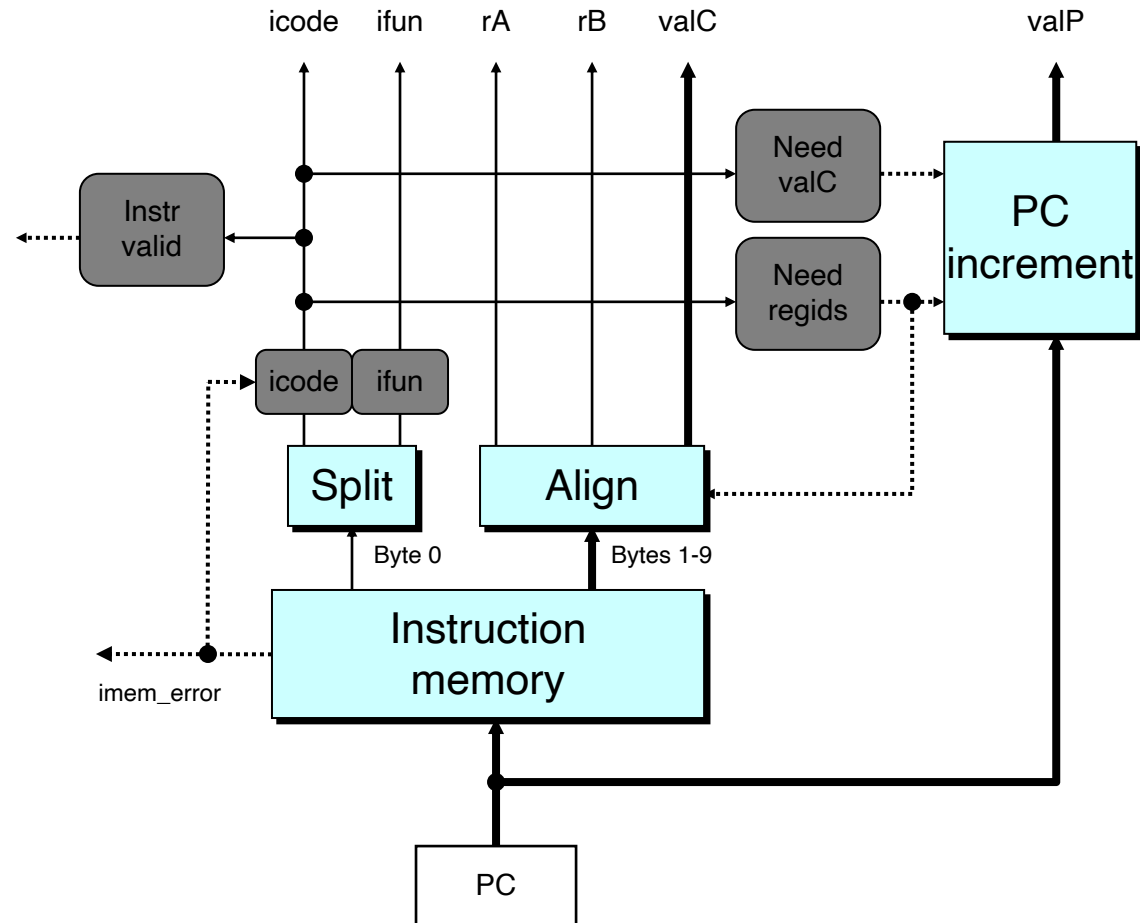


## ■ Control Logic

- **Instr. Valid:** Is this instruction **valid**?
- **icode, ifun:** Generate no-op if invalid address
- **Need regids:** Does this instruction have a register byte?
- **Need valC:** Does this instruction have a constant word?


# Fetch Control Logic in HCL

```
# Determine instruction code
int icode = [
    imem_error: INOP;
    1: imem_icode;
];
 
# Determine instruction function
int ifun = [
    imem_error: FNONE;
    1: imem_ifun;
];
```



# Fetch Control Logic in HCL

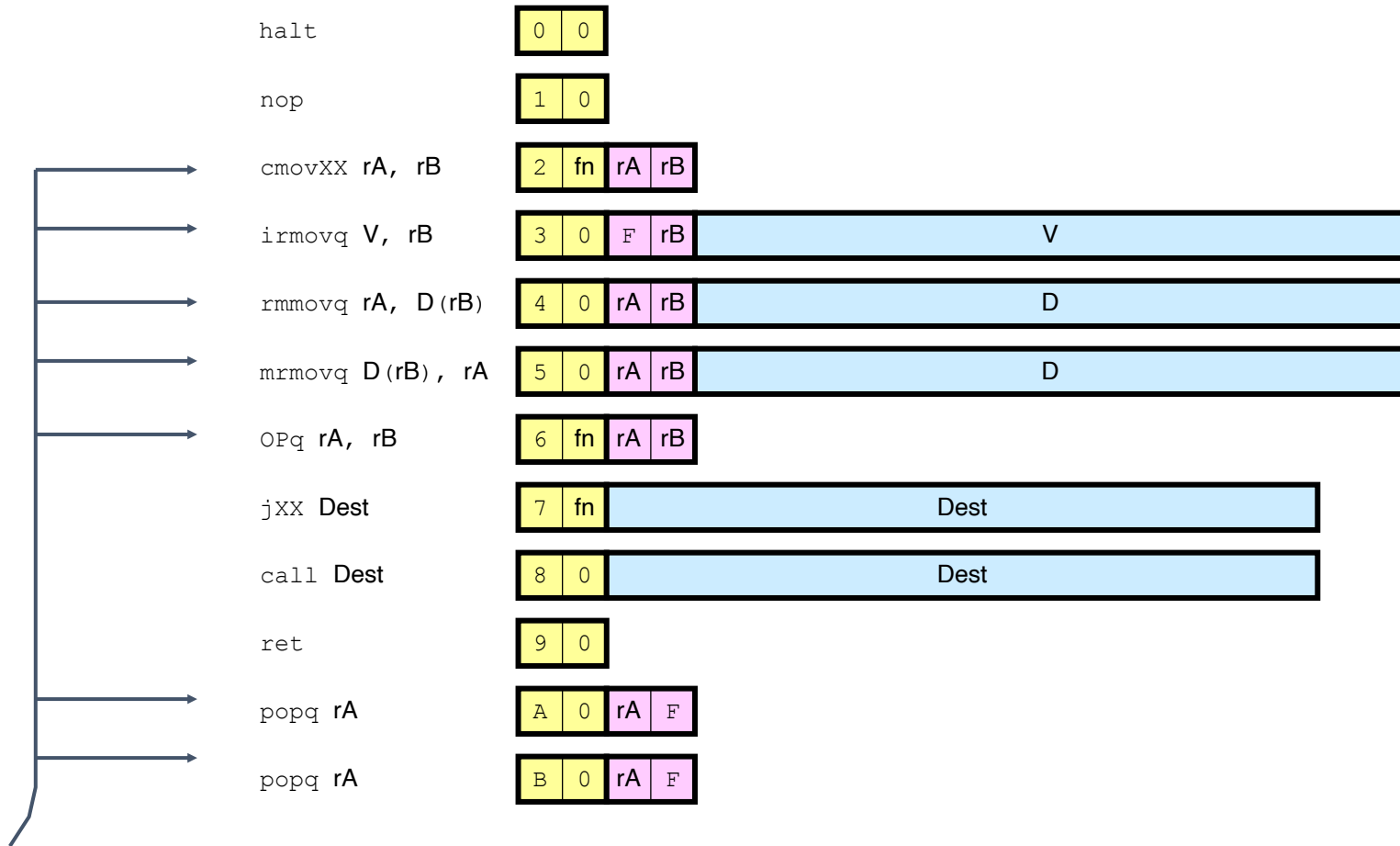

```
bool need_regids =  
    icode in { IRRMOVQ, IOPQ, IPUSHQ, IPOPQ,  
              IIRMOVQ, IRMMOVQ, IMRMOVQ };
```

```
bool instr_valid = icode in  
    { INOP, IHALT, IRRMOVQ, IIRMOVQ, IRMMOVQ, IMRMOVQ,  
      IOPQ, IJXX, ICALL, IRET, IPUSHQ, IPOPQ };
```

# Quiz Time!

**Exercise 4.19**

# Decode Logic

## ■ Register File


- Read ports A, B
- Write ports E, M
- Addresses are register IDs or 15 (0xF) (no access)

## ■ Control Logic

- **srcA, srcB**: read port addresses for valA, valB
- **dstE, dstM**: write port addresses for valE, valM
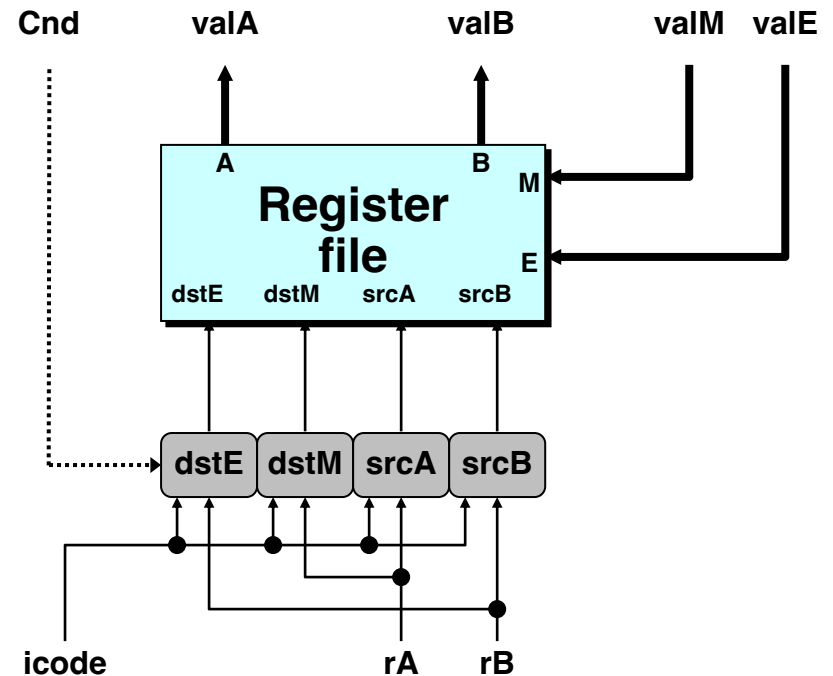
## ■ Signal

- **Cnd**: Indicate whether or not to perform **conditional move**
- Computed in Execute stage



# A Source

	OPq rA, rB	
Decode	valA ← R[rA]	Read operand A
	cmovXX rA, rB	
Decode	valA ← R[rA]	Read operand A
	rmmovq rA, D(rB)	
Decode	valA ← R[rA]	Read operand A
	popq rA	
Decode	valA ← R[%rsp]	Read stack pointer
	jXX Dest	
Decode		No operand
	call Dest	
Decode		No operand
	ret	
Decode	valA ← R[%rsp]	Read stack pointer

```
int srcA = [  
    icode in { IRRMOVQ, IRMMOVQ, IOPQ, IPUSHQ } : rA;  
    icode in { IPOPOPQ, IRET } : RRSP;  
    1 : RNONE; # Don't need register  
];
```

# Quiz Time!

**Exercise 4.20**

**Please refer Figure 4-18 ~ 4-21.**

# E Destination

	OPq rA, rB	
Write-back	R[rB] ← valE	Write back result
	cmovXX rA, rB	
Write-back	R[rB] ← valE	Conditionally write back result
	rmmovq rA, D(rB)	
Write-back		None
	popq rA	
Write-back	R[%rsp] ← valE	Update stack pointer
	jXX Dest	
Write-back		None
	call Dest	
Write-back	R[%rsp] ← valE	Update stack pointer
	ret	
Write-back	R[%rsp] ← valE	Update stack pointer

```
int dstE = [
    icode in { IRRMOVQ } && Cnd : rB;
    icode in { IIRMOVQ, IOPQ } : rB;
    icode in { IPUSHQ, IPOPOPQ, ICALL, IRET } : RRSP;
    1 : RNONE; # Don't write any register
];
```



# Execute Logic

## ■ Units

### ■ ALU

- Implements 4 required functions
- Generates condition code values

### ■ CC


- Register with 3 condition code bits

### ■ cond

- Computes conditional jump/move flag
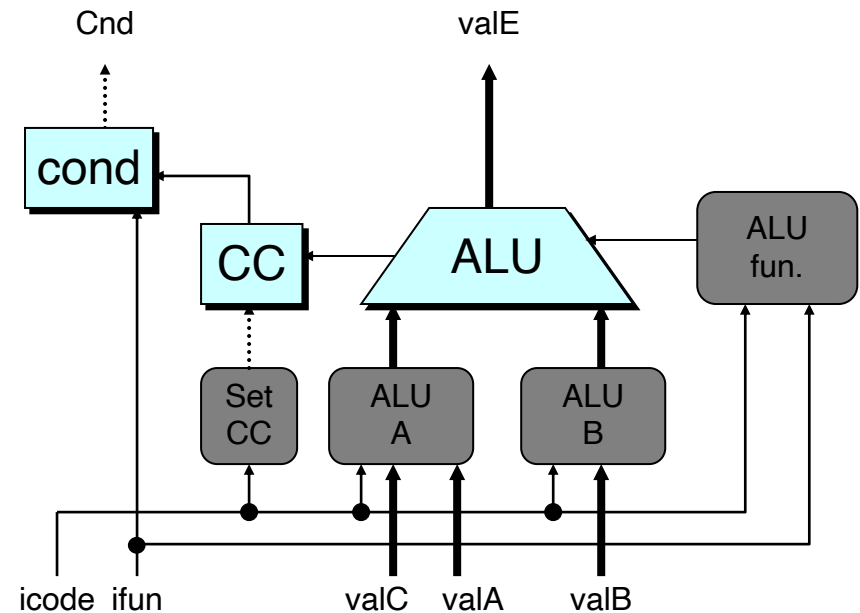
## ■ Control Logic

- Set CC: Should condition code register be loaded?
- ALU A: Input A to ALU
- ALU B: Input B to ALU
- ALU fun: What function should ALU compute?



# ALU A Input

	OPq rA, rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	cmovXX rA, rB	
Execute	$valE \leftarrow 0 + valA$	Pass valA through ALU
	rmmovq rA, D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popq rA	
Execute	$valE \leftarrow valB + 8$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -8$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 8$	Increment stack pointer

```
int aluA = [  
    icode in { IRRMOVQ, IOPQ } : valA;  
    icode in { IIRMOVQ, IRMMOVQ, IMRMOVQ } : valC;  
    icode in { ICALL, IPUSHQ } : -8;  
    icode in { IRET, IPOPQ } : 8;  
    # Other instructions don't need ALU  
];
```

# ALU Operation

	OPI rA, rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	cmovXX rA, rB	
Execute	$valE \leftarrow 0 + valA$	Pass valA through ALU
	rmmovl rA, D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popq rA	
Execute	$valE \leftarrow valB + 8$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -8$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 8$	Increment stack pointer

```
int alufun = [  
    icode == IOPQ : ifun;  
    1 : ALUADD;  
];
```

# Quiz Time!

## Exercise 4.23


# Memory Logic

## ■ Memory

- Reads or writes memory word
 
## ■ Control Logic


- stat: What is instruction status?
- Mem. read: should word be read?
- Mem. write: should word be written?
- Mem. addr.: Select address
- Mem. data.: Select data



# Instruction Status

## Control Logic

- stat: What is instruction status?

 

```
## Determine instruction status
int Stat = [
    imem_error || dmem_error : SADR;
    !instr_valid: SINS;
    icode == IHALT : SHLT;
    1 : SAOK;
];
```

# Memory Read

Memory	OPq rA, rB	No operation
Memory	mrmovq D(rB), rA $valE \leftarrow M_8[valE]$	Write value to memory
Memory	popq rA $valM \leftarrow M_8[valA]$	Read from stack
Memory	jXX Dest	No operation
Memory	call Dest $M_8[valE] \leftarrow valP$	Write return value on stack
Memory	ret $valM \leftarrow M_8[valA]$	Read return address

```
bool mem_read = icode in { IMRMOVQ, IPOPOPQ, IRET };
```

# Memory Address

Memory	OPq rA, rB	No operation
Memory	rmmovq rA, D(rB) $M_8[\text{valE}] \leftarrow \text{valA}$	Write value to memory
Memory	popq rA $\text{valM} \leftarrow M_8[\text{valA}]$	Read from stack
Memory	jXX Dest	No operation
Memory	call Dest $M_8[\text{valE}] \leftarrow \text{valP}$	Write return value on stack
Memory	ret $\text{valM} \leftarrow M_8[\text{valA}]$	Read return address

```
int mem_addr = [  
    icode in { IRMMOVQ, IPUSHQ, ICALL, IMRMOVQ } : valE;  
    icode in { IPOPOPQ, IRET } : valA;  
    # Other instructions don't need address  
];
```




# Quiz Time!

Exercise 4.25

# PC Update Logic

- **New PC**
  - Select next value of PC

 


# PC Update

	OPq rA, rB	
PC update	PC ← valP	Update PC
	rmmovq rA, D(rB)	
PC update	PC ← valP	Update PC
	popq rA	
PC update	PC ← valP	Update PC
	jXX Dest	
PC update	PC ← Cnd ? valC : valP	Update PC
	call Dest	
PC update	PC ← valC	Set PC to destination
	ret	
PC update	PC ← valM	Set PC to return address

```
int new_pc = [  
    icode == ICALL : valC;  
    icode == IJXX && Cnd : valC;  
    icode == IRET : valM;  
    1 : valP;  
];
```

# SEQ Operation

 

## ■ State


- PC register
- Cond. Code register
- Data memory
- Register file

*All updated as clock rises*


## ■ Combinational Logic

- ALU
- Control logic
- Memory reads
  - Instruction memory
  - Register file
  - Data memory

# SEQ Operation #2

 


Cycle 1:	0x000:	<code>irmovq \$0x100,%rbx</code>	# %rbx <-- 0x100
Cycle 2:	0x00a:	<code>irmovq \$0x200,%rdx</code>	# %rdx <-- 0x200
Cycle 3:	0x014:	<code>addq %rdx,%rbx</code>	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	<code>je dest</code>	# Not taken
Cycle 5:	0x01f:	<code>rmmovq %rbx,0(%rdx)</code>	# M[0x200] <-- 0x300

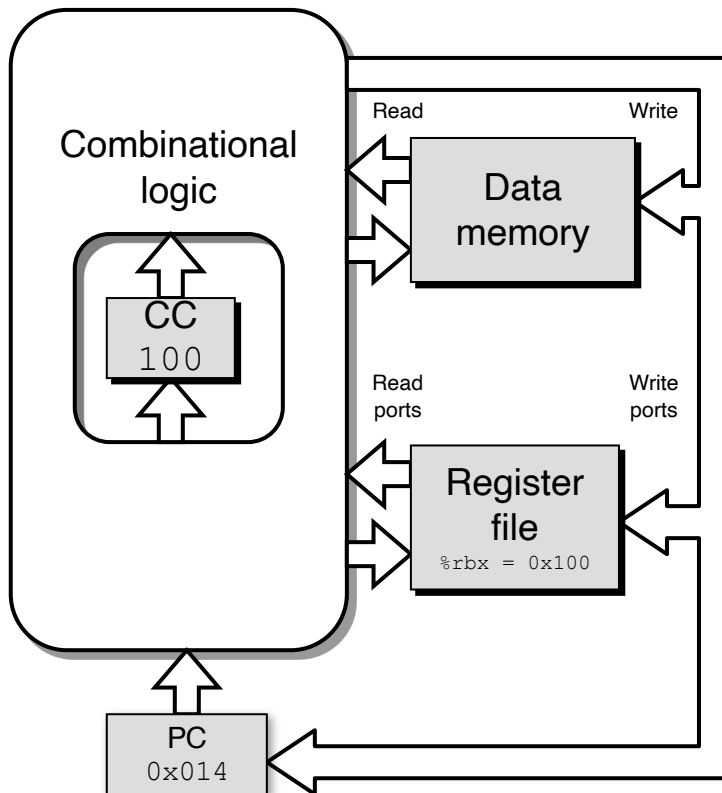


- state set according to second `irmovq` instruction
- combinational logic starting to react to state changes

# SEQ Operation #3

 


Cycle 1:	0x000:	irmovq \$0x100,%rbx	# %rbx <-- 0x100
Cycle 2:	0x00a:	irmovq \$0x200,%rdx	# %rdx <-- 0x200
Cycle 3:	0x014:	addq %rdx,%rbx	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	je dest	# Not taken
Cycle 5:	0x01f:	rmmovq %rbx,0(%rdx)	# M[0x200] <-- 0x300

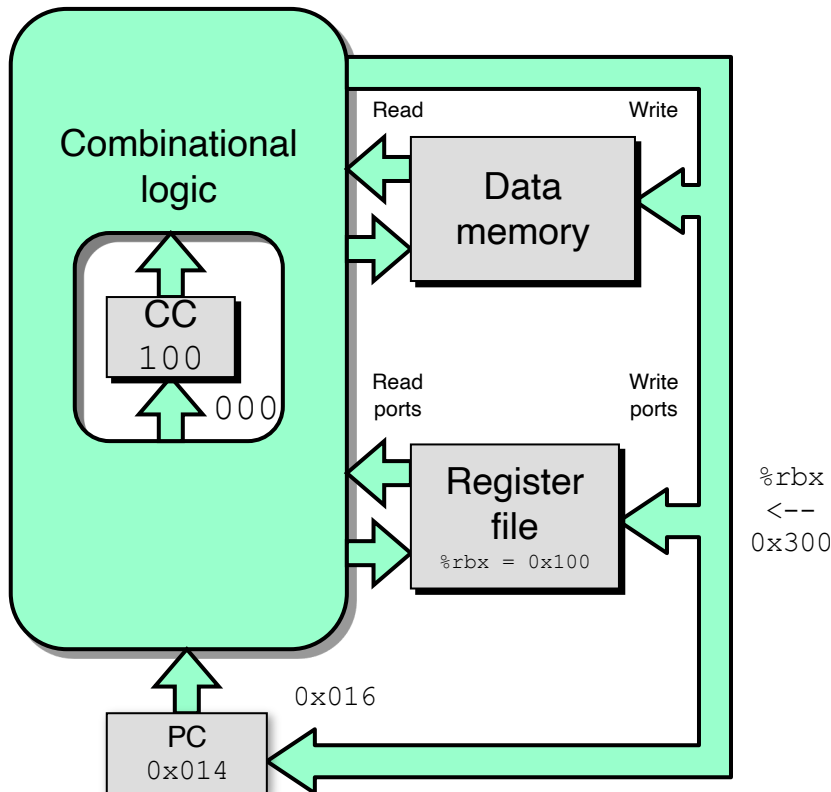


- state set according to second `irmovq` instruction
- combinational logic generates results for `addq` instruction

# SEQ Operation #4

 


Cycle 1:	0x000:	irmovq \$0x100,%rbx	# %rbx <-- 0x100
Cycle 2:	0x00a:	irmovq \$0x200,%rdx	# %rdx <-- 0x200
Cycle 3:	0x014:	addq %rdx,%rbx	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	je dest	# Not taken
Cycle 5:	0x01f:	rmmovq %rbx,0(%rdx)	# M[0x200] <-- 0x300

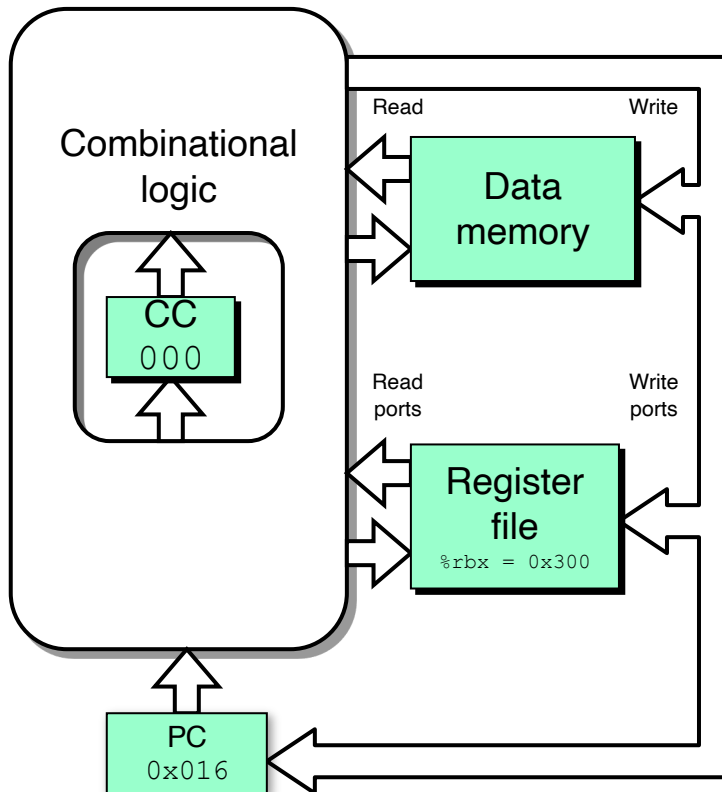


- state set according to addq instruction
- combinational logic starting to react to state changes

# SEQ Operation #5

 

Cycle 1:	0x000:  irmovq \$0x100,%rbx  # %rbx <-- 0x100
Cycle 2:	0x00a:  irmovq \$0x200,%rdx  # %rdx <-- 0x200
Cycle 3:	0x014:  addq %rdx,%rbx      # %rbx <-- 0x300  CC <-- 000
Cycle 4:	0x016:  je dest            # Not taken
Cycle 5:	0x01f:  rmmovq %rbx,0(%rdx) # M[0x200] <-- 0x300

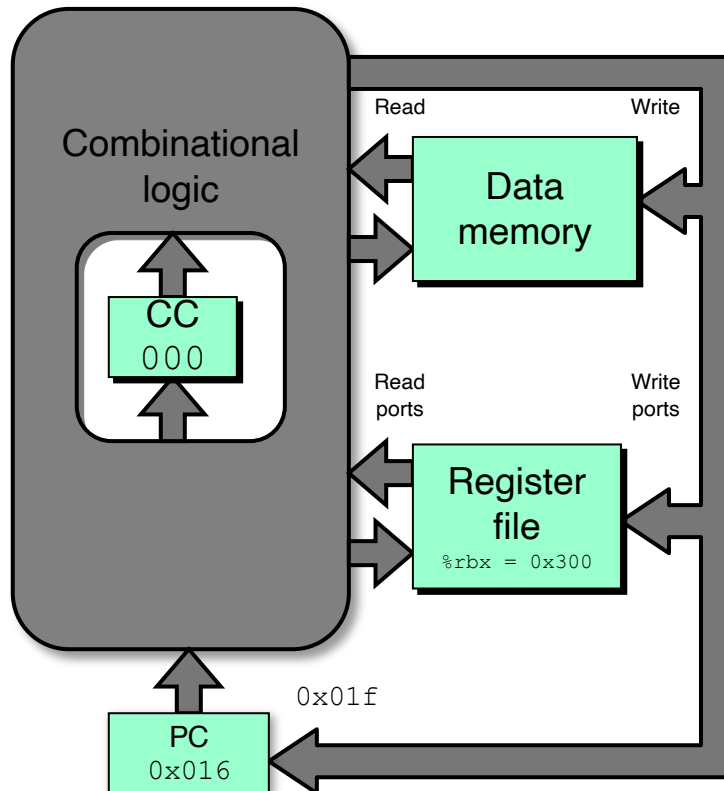

- state set according to addq instruction
- combinational logic generates results for je instruction



# SEQ Summary

## ■ Implementation

- Express every instruction as series of simple steps
- Follow same general flow for each instruction type
- Assemble registers, memories, predesigned combinational blocks
- Connect with control logic

## ■ Limitations

- Too slow to be practical
- In one cycle, must propagate through instruction memory, register file, ALU, and data memory
- Would need to **run clock very slowly**
- **Hardware units only active for fraction of clock cycle**